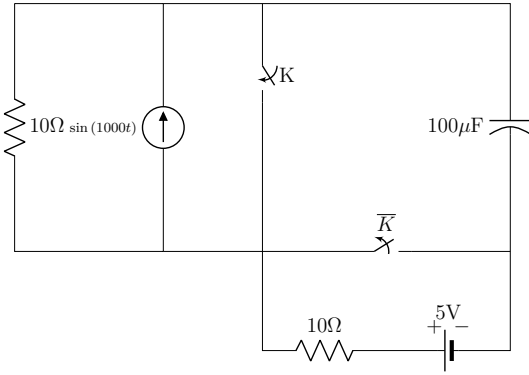



EE23BTECH11054 - Sai Krishna Shanigarapu*

GATE EE 2023

54. The circuit shown in the figure is initially in the steady state with the switch K in open condition and \overline{K} in closed condition. The switch K is closed and \overline{K} is opened simultaneously at the instant $t = t_1$, where $t_1 > 0$. The minimum value of t_1 in milliseconds such that there is no transient in the voltage across the $100 \mu F$ capacitor, is _____ (Round off to 2 decimal places).

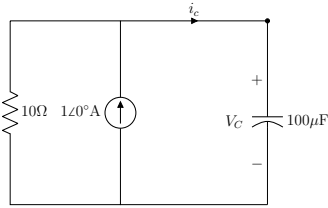**Solution:**

Case(i) Switch K is open and \overline{K} is closed.



$$X_c = -10j \quad (1)$$

Using Current divider rule,

$$i_c = \frac{10}{10 + X_c} 1\angle 0^\circ \quad (2)$$


$$= \frac{1\angle 0^\circ}{1 - j} \quad (3)$$

$$V_c = i_c X_c \quad (4)$$

$$= 7.07\angle -45^\circ V \quad (5)$$

$$\Rightarrow V_c = 7.07 \sin(1000t - 45^\circ) V \quad (6)$$

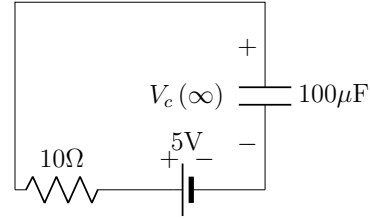Case(ii) Switch K is closed and \overline{K} is open.



Symbol	description	value
$V_C(\infty)$	Voltage across capacitor after long time	5V
τ	Time constant	1 msec
R	Resistance	10Ω
C	capacitance	100μF

TABLE I
PARAMETERS

From Table I and Table II,

$$V_c(t) = 5 + (7.07 \sin(100t - 45^\circ) - 5) e^{-(t-t_1)/\tau} \quad (7)$$

For transient free voltage,

$$7.07 \sin(100t_1 - 45^\circ) = 5 \quad (8)$$

$$1000t_1 - \frac{\pi}{4} = \frac{5}{7.07} \quad (9)$$

$$\Rightarrow t_1 \approx 1.57 \text{ msec} \quad (10)$$

Symbol	Description	Formula
τ	Time constant	RC
$V_c(t)$	Voltage across capacitor at time t	$V_c(\infty) + (V_c(0) - V_c(\infty)) e^{-t/\tau}$

TABLE II
FORMULAE